

Experiment - 2

9/45 - 11/45

PAGE NO.: 1
DATE: 15/9/23



Aim:- To Perform and Solve Electrical Network with Series and Parallel Combinations of Resistors Using Kirchhoff's Laws.

(A)

For KVL [Kirchhoff's Voltage Law]

APPARATUS:

Sr No.	Equipment Name	Range	Quantity
1	Voltage Source	0 - 20V	1
2	Voltmeter	0 - 20V	3
3	Ammeter	0 - 200mA	1
4	Resistors	2.2 kΩ 1 kΩ	12
5	Patch cord	-	as per requirement

88.1

08.0

8.0

VS

82.8

81.1

0.1

VA

10.11

88.1

88.1

VA

2.2


2.5

H.S

VA

2011-2012
S.S.

S - Manisha

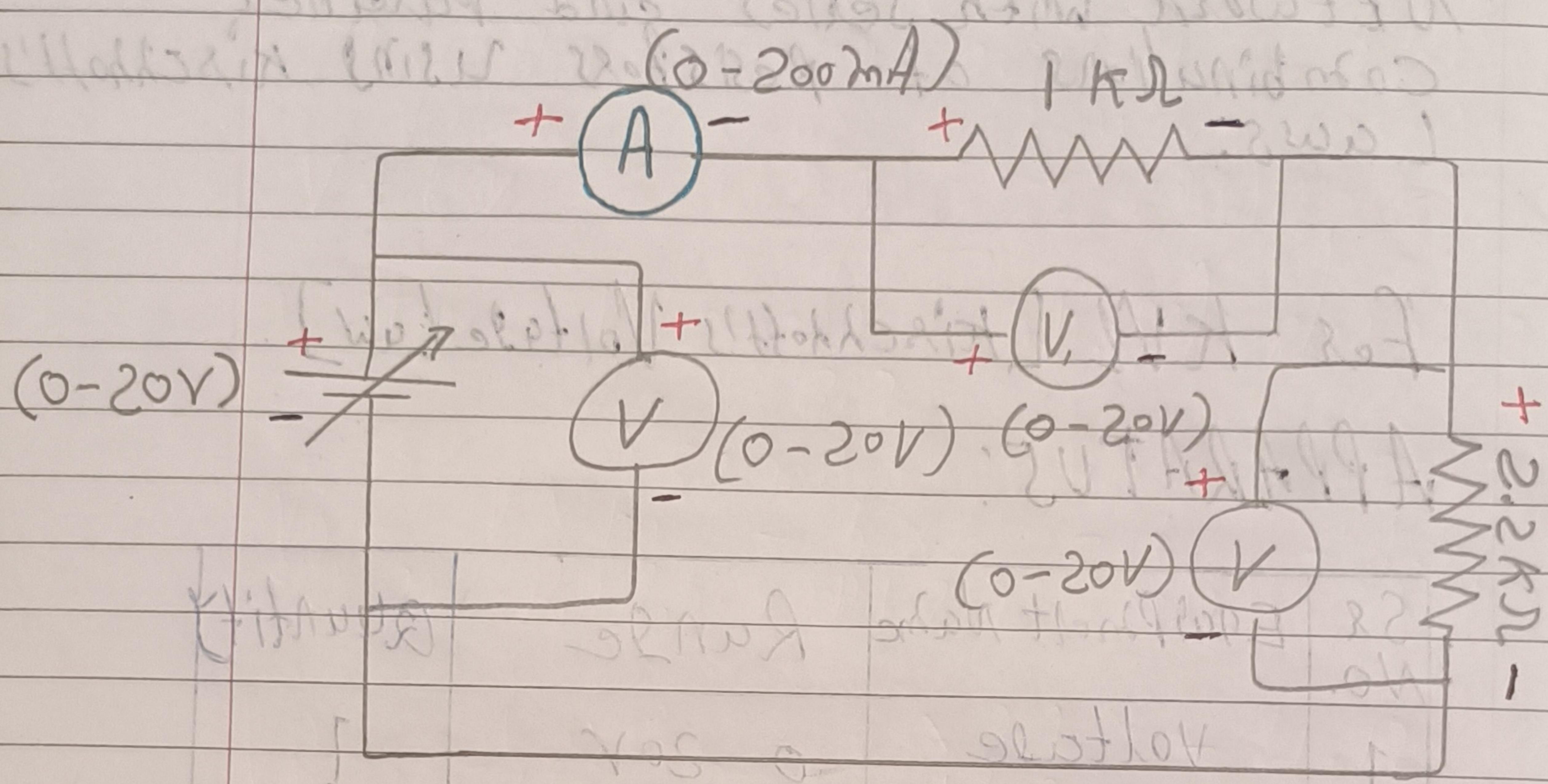Circuit DiagramObservation Table:-

Sl No.	Supply Voltage V_s (Volts)	Current I (mA)	Voltage across R_1 V_{R_1} (Volts)	Voltage across R_2 V_{R_2} (Volts)
1	2V	0.6	0.80	1.37
2	4V	1.0	1.18	2.88
3	6V	1.86	1.86	4.08
4	8V	2.4	2.5	5.5

calculation

V = 2V Voltage Divider rule [VDR]

$$R_{eq} = R_1 + R_2$$

$$= 1k\Omega + 2.2k\Omega \\ = 3.2k\Omega$$

$$I_1 = \frac{V}{R_{eq}} = \frac{2}{3.2} = 0.6mA$$

$$V_{R_1} = \frac{V \times R_1}{R_1 + R_2} = \frac{2 \times 1}{1 + 2.2} = \frac{2}{3.2} = 0.6V$$

$$V_{R_2} = \frac{2 \times 2.2}{3.2} = 1.32V$$


V = 4V

$$R_{eq} = R_1 + R_2$$

$$= 1k\Omega + 2.2k\Omega \\ = 3.2k\Omega$$

$$I_2 = \frac{V}{R_{eq}} = \frac{4}{3.2} = 1.25mA$$

$$V_{R_1} = \frac{V \times R_1}{R_1 + R_2} = \frac{4 \times 1}{1 + 2.2} = \frac{4}{3.2} = 1.25V$$

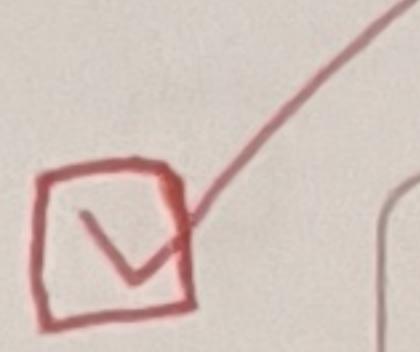PAGE NO.: u

DATE: / /

$$V_{R_2} = \frac{V \times R_2}{R_1 + R_2} = \frac{4 \times 2.2}{1 + 2.2} = 2.75 V$$

$$\underline{V = 6 V}$$

$$I_3 = \frac{V}{R_{eq}} = \frac{6}{3.2} = 1.87 A$$

$$V_{R_1} = \frac{V \times R_1}{R_1 + R_2} = \frac{6 \times 1}{1 + 2.2} = \frac{6}{3.2} = 1.87 V$$


$$V_{R_2} = \frac{V \times R_2}{R_1 + R_2} = \frac{6 \times 2.2}{1 + 2.2} = 4.12 V$$

$$\underline{V = 8 V}$$

$$I_4 = \frac{V}{R_{eq}} = \frac{8}{3.2} = 2.5 A$$

$$V_{R_1} = \frac{V \times R_1}{R_1 + R_2} = \frac{8 \times 1}{1 + 2.2} = \frac{8}{3.2} = 2.5 V$$
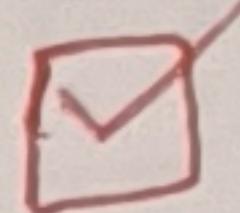
$$V_{R_2} = \frac{V \times R_2}{R_1 + R_2} = \frac{8 \times 2.2}{3.2} = 5.5 V$$




For KCL [Kirchhoff's Current Law]


APPARATUS

S.R. No.	Equipment Name	Range	Quantity
1	Voltage source	0 - 20V	1
2	Voltmeter	0 - 20V	3
3	Ammeter	0 - 200mA	3
4	Resistor	2.2 kΩ 1 kΩ	1
5	Patch cord	-	as per require

Circuit Diagram

*[Not mandatory]

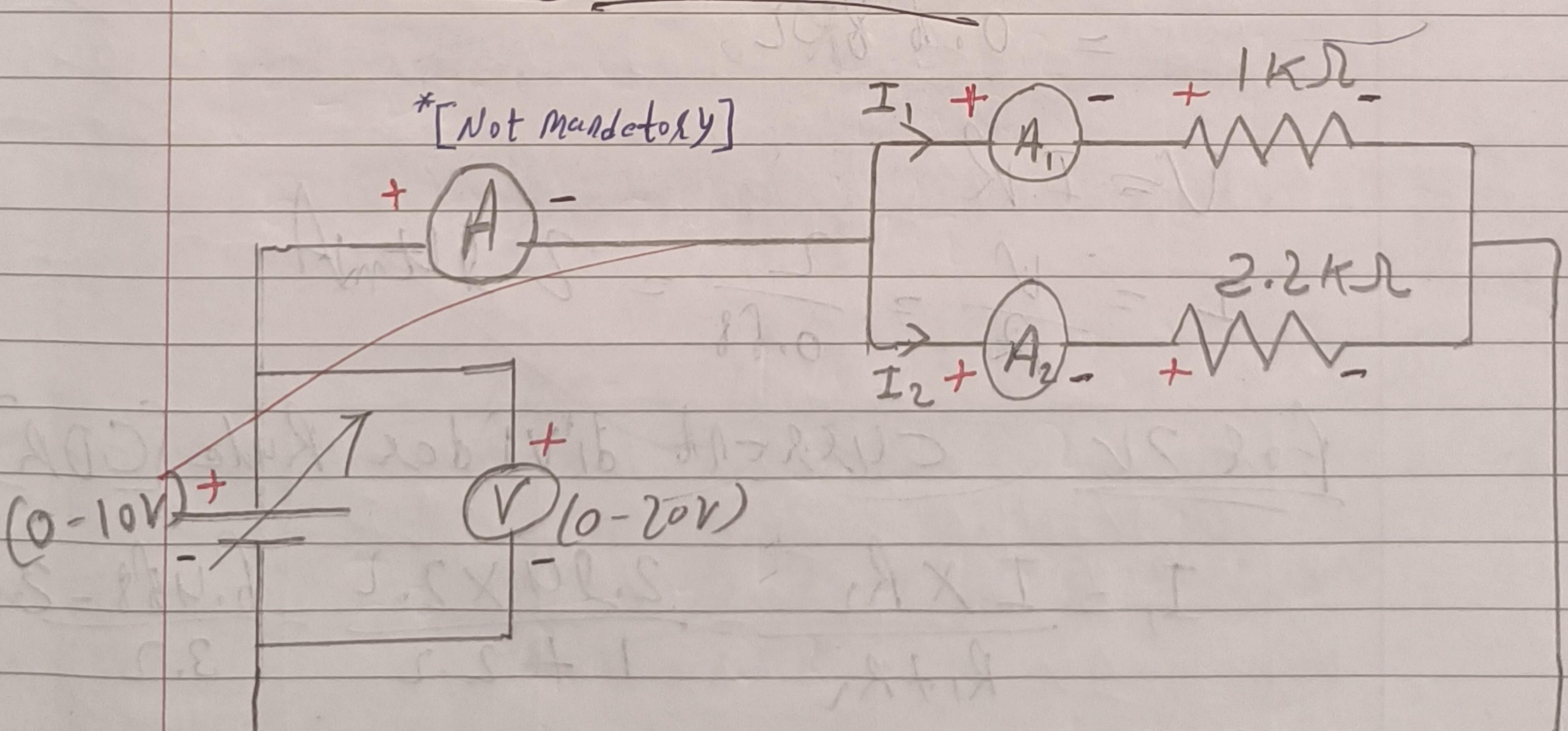

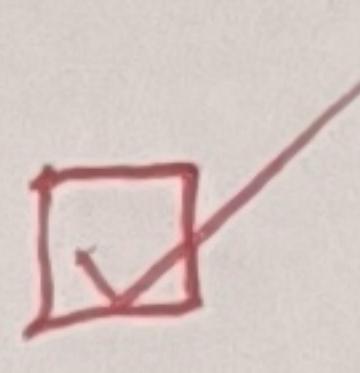Observation table

SNo	SUPPLY Voltage [Vs]	current through 1 kΩ (I ₁)	current through 2.2 kΩ (I ₂)	total current I = I ₁ + I ₂
1	2V	2.0 mA	0.9 mA	2.0 + 0.9 = 2.9
2	5V	5.1 mA	2.4 mA	5.1 + 2.4 = 7.4
3	2V	6.5 mA	3.3 mA	6.5 + 3.3 = 10.2

Calculation


$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 \cdot R_2}{R_1 + R_2} = \frac{1 \times 2.2}{1 + 2.2} = \frac{2.2}{3.2} = 0.68 \text{ k}\Omega$$

$$V = IR$$

$$I = \frac{V}{R} = \frac{2}{0.68} = 2.94 \text{ mA}$$

For 2V Current divider Rule [CDR]
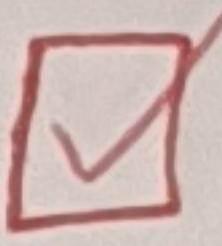
$$I_1 = \frac{I \times R_1}{R_1 + R_2} = \frac{2.94 \times 2.2}{1 + 2.2} = \frac{6.488}{3.2} = 2 \text{ mA}$$



$$I_2 = \frac{I \times R_1}{R_1 + R_2} = \frac{2.94 \times 1}{3.2} = 0.94 \text{ mA}$$

$$I = I_1 + I_2 = 2 + 0.94 = 2.94 \text{ mA}$$

for 5V

$$I = \frac{V}{R_{\text{ext}}} = \frac{5}{0.68} = 7.3 \text{ mA}$$

$$I_1 = \frac{I \times R_1}{R_1 + R_2} = \frac{7.3 \times 2.2}{1 + 2.2} = \frac{16.06}{3.2} = 5 \text{ mA}$$

$$I_2 = \frac{I \times R_2}{R_1 + R_2} = \frac{7.3 \times 1}{1 + 2.2} = \frac{7.3}{3.2} = 2.2 \text{ mA}$$

$$I = I_1 + I_2 = 5 + 2.2 = 7.2 \text{ mA}$$


for 7V

$$I = \frac{V}{R_{\text{ext}}} = \frac{7}{0.68} = 10.29 \text{ mA}$$

$$I_1 = \frac{I \times R_1}{R_1 + R_2} = \frac{10.29 \times 2.2}{1 + 2.2} = 7.07 \text{ mA}$$

$$I_2 = \frac{I \times R_2}{R_1 + R_2} = \frac{10.29 \times 1}{1 + 2.2} = 3.21 \text{ mA}$$

$$I = I_1 + I_2 = 7.07 + 3.21 = 10.28$$

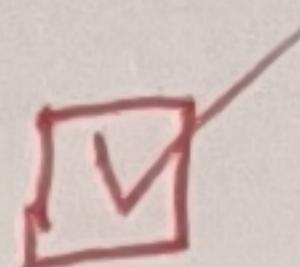

PAGE NO.: 9

DATE: / /


Conclusion [For KVL] :- After performing experiment we verified the Kirchoff's Voltage Law with the help of two series resistance. The calculate resistance value for the two resistance were found to be same as we calculated.

Conclusion [For KCL] :- After performing this experiment we can verify the KCL with help of parallel resistor. The calculated total resistance of the circuit using the formula was to be appear same to the reading performed during the experiment.

S.R No.	Current due to gr [I'] supply Voltage (V) (mA)	Current due to gr (I) (mA)	Current due to gr [I''] (mA)	Total current $I = I' + I''$ (mA)
1	9V	2.14	-	$2.14 + 0.86$
2	5V	-	0.54	-

Experiment - 3

PAGE NO.: 9
DATE: / /

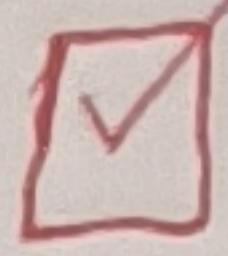


Aim:- To Verify superposition theorem.


Apparatus:-

Sr.no.	Equipment Name	Range	Quantity
1.	DC SUPPLY	9V	1
2	Voltmeter (0-20V)	5V	1
3	Ammeter (0-200mA)	(0-200mA)	1
4	Resistances	1kΩ 2.2kΩ	1
5	Patch cords	As Per Required	
6	Power cord		1

Circuit Diagram

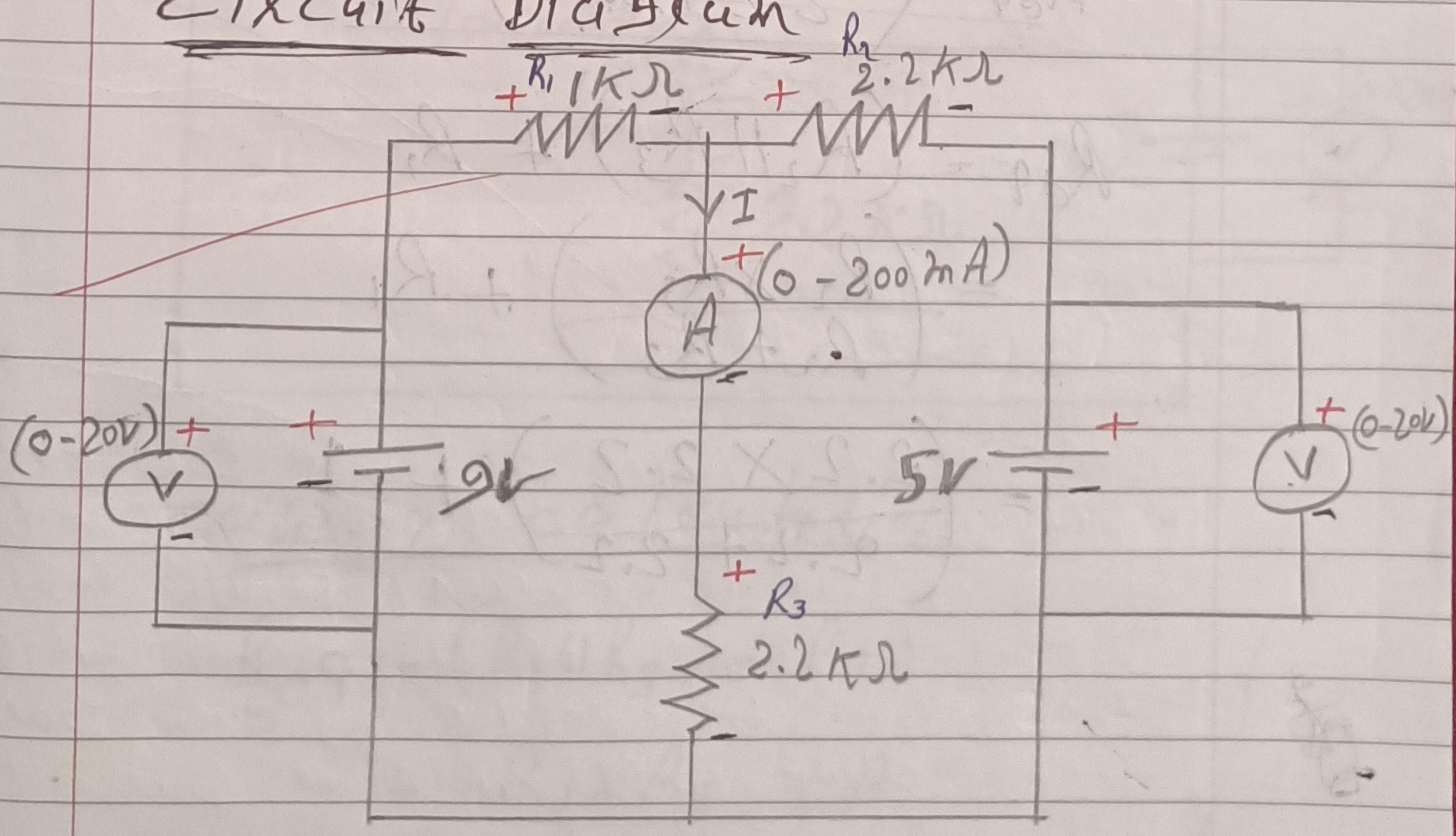

E - Electronics

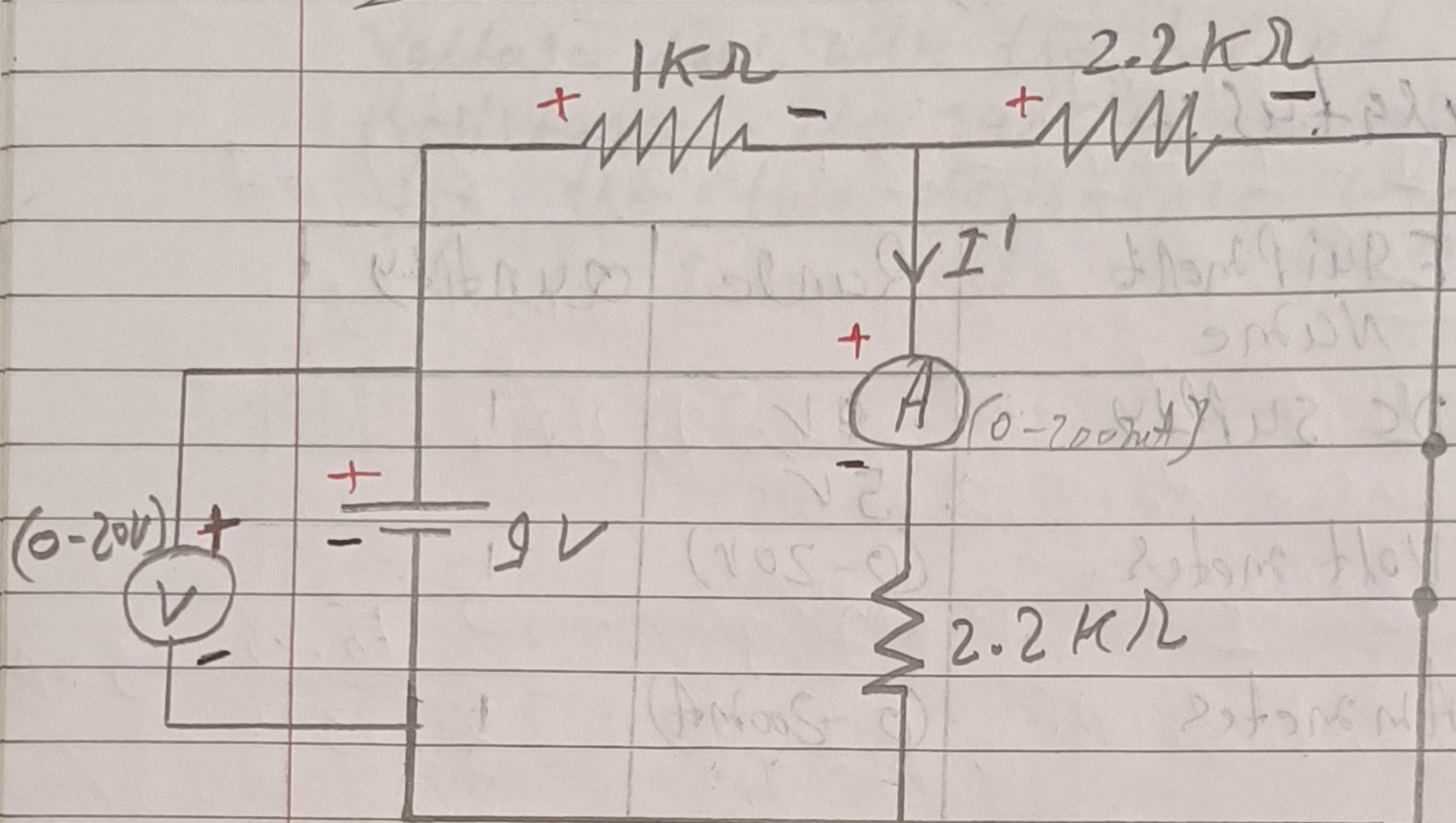
Case - 1case-1 calculation

$$R_{eq} = \left(\frac{2.2 \times 2.2}{2.2 + 2.2} \right) + 1$$

$$\begin{aligned} R_{eq} &= (R_2 || R_3) + R_1 \\ &= \left(\frac{R_2 \times R_3}{R_2 + R_3} \right) + R_1 \end{aligned}$$

$$= \left(\frac{2.2 \times 2.2}{2.2 + 2.2} \right) + 1$$

Ans

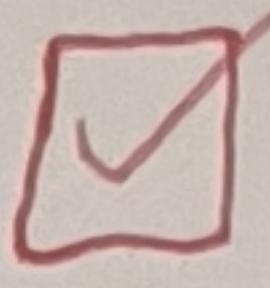

Observation table


Volt across (R _S)	Current through series (I ₁ , I ₂)	Current across testor (I ₁ ', I ₂ ')
3V	I ₁ = 3.12 mA	I ₁ ' = 0.92 mA
5V	I ₂ = 2.38 mA	I ₂ ' = 1.13 mA

$$= \frac{4.84}{4.4} + 1 \\ = 1.1 + 1 \\ \boxed{R_{eq} = 2.1 \Omega}$$

$$I_1 = \frac{9}{2.1} = 4.28 \text{ mA}$$

$$I_1 = \frac{4.28 \times 2.2}{4.4} = \frac{9.416}{4.4} = 2.14 \text{ mA}$$

case - 2

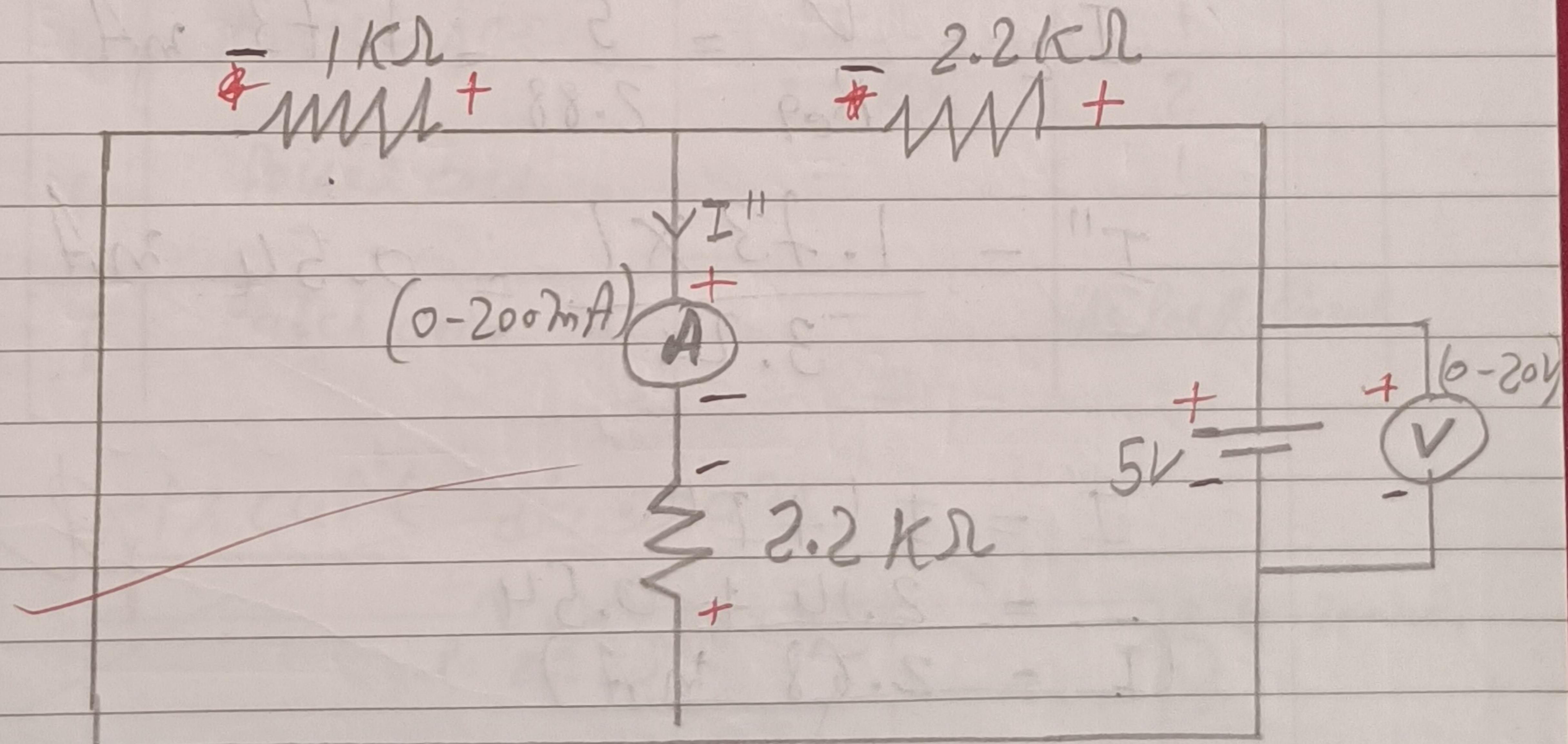

case - 2 calculation

$$R_{eq} = (R_1 || R_3) + R_2$$

$$= \frac{R_1 \times R_3}{R_1 + R_3} + R_2$$

$$= \left(\frac{1 \times 2.2}{1 + 2.2} \right) + 2.2$$

$$= \left(\frac{2.2}{3.2} \right) + 2.2$$

$$= 0.68 + 2.2$$

$$R_{eq} = 2.88 \Omega$$

$$I_2 = \frac{V}{R_{eq}} = \frac{5}{2.88} = 1.73 \text{ mA}$$

$$I'' = \frac{1.73 \times 1}{3.2} = 0.54 \text{ mA}$$

$$\begin{aligned} I &= I' + I'' \\ &= 2.14 + 0.54 \\ (I &= 2.68 \text{ mA}) \end{aligned}$$

Conclusion:- After performing this experiment we have verified the superposition theorem by showing that the current through resistor is equal to the sum of the current that passed through that resistor by each source acting alone with an other source turned off.

Experiment - 4

PAGE NO.: 13


DATE:

Aim:- To Validation of Thevenin theorem,

Apparatus :-

Sl No.	Equipment Name	Range	Quantity
1	DC Voltmeter (0-20V)	1	1
2	DC Ammeter (0-200mA)	1	1
3	DC Power Supply (0-10V)	1	1
4	Resistance	1kΩ 2.2kΩ	1 2
5	Power cord	-	1
6	Patch cord	-	As Per Required

Circuit diagram

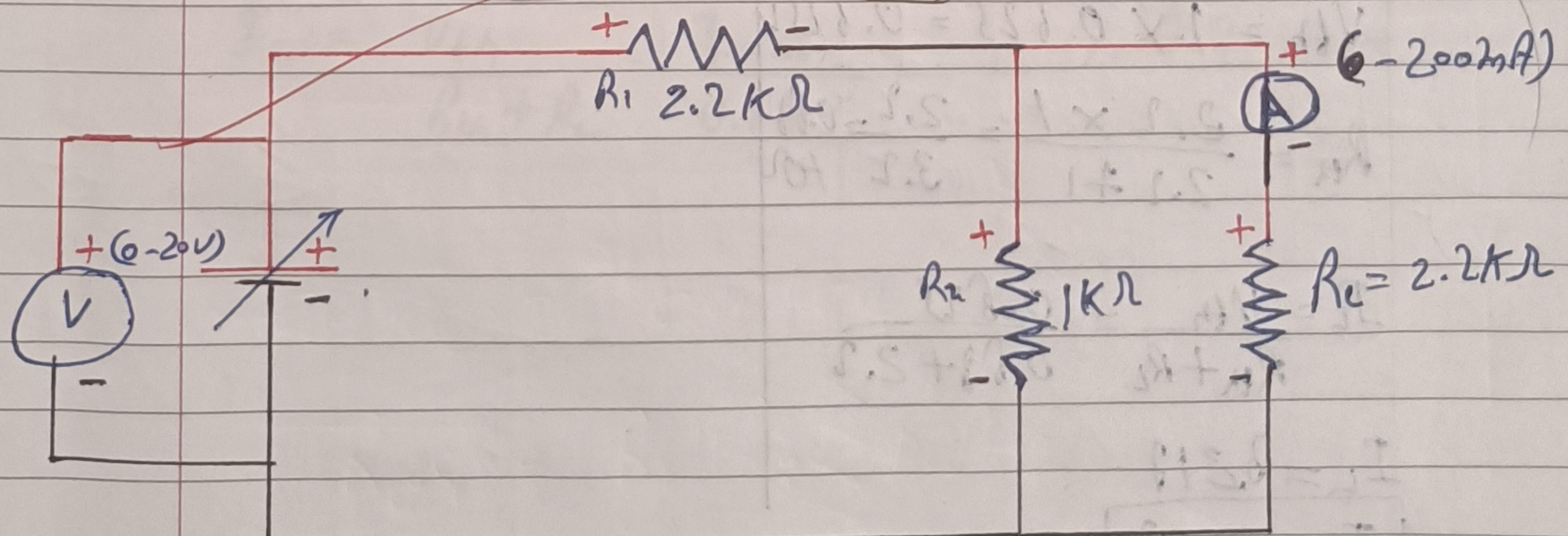

other two circuits →

Observation table

S.R No.	SUPPLY Voltage _s [V _s]	V _{th}	R _{th}	I _L
1	2V	0.625V	0.68Ω	0.22mA
2	5V	1.5V	0.68V	0.52mA
3	7V	2.10V	0.68V	0.77mA
4	9V	2.81V	0.68V	0.98mA

Calculation

For V_{th}

1)

2V

$$I = \frac{V}{R_{eq}} = \frac{2}{3.2} = 0.625$$

~~$$R_{eq} = R_{TH} = \frac{2.2 \times 1}{2.2 + 1}$$~~

~~$$= R_1 + R_2 = 2.2 + 1$$~~

~~$$R_{eq} = 3.2 \Omega$$~~

$$V_{th} = 1 \times 0.625 = 0.625V$$

$$R_{th} = \frac{2.2 \times 1}{2.2 + 1} = \frac{2.2}{3.2} = 0.68 \Omega$$

$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{0.625}{0.68 + 2.2}$$

$$I_L = 0.218$$

$$\boxed{I_L = 0.22}$$

ii) 5V

$$I = \frac{V}{R_{eq}} = \frac{5}{3.2} = 1.5 \text{ mA}$$

$$V_{th} = I \times 1.5 = 1.5 \text{ V}$$

$$R_{th} = \frac{2.2 \times 1}{2.2 + 1} = \frac{2.2}{3.2} = 0.68 \text{ k}\Omega$$

$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{1.5}{0.68 + 2.2} = \frac{1.5}{2.88} = 0.52 \text{ mA}$$

iii) 7V

$$I = \frac{V}{R_{eq}} = \frac{7}{3.2} = 2.19 \text{ mA}$$

~~$$V_{th} = I \times 2.19 = 2.19 \text{ V}$$~~

~~$$R_{th} = \frac{2.2 \times 1}{2.2 + 1} = \frac{2.2}{3.2} = 0.68 \text{ k}\Omega$$~~

$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{2.19}{0.68 + 2.2} = 0.77 \text{ mA}$$

ix) 9V


$$I = \frac{V}{R_{th}} = \frac{9}{3.2} = 2.81 \text{ mA}$$

$$V_{th} = 1 \times 2.81 = 2.81 \text{ V}$$

$$R_{th} = \frac{2.2 \times 1}{2.2 + 1} = \frac{2.2}{3.2} = 0.68 \text{ k}\Omega$$

$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{2.81}{0.68 + 2.2} = 0.98 \text{ mA}$$

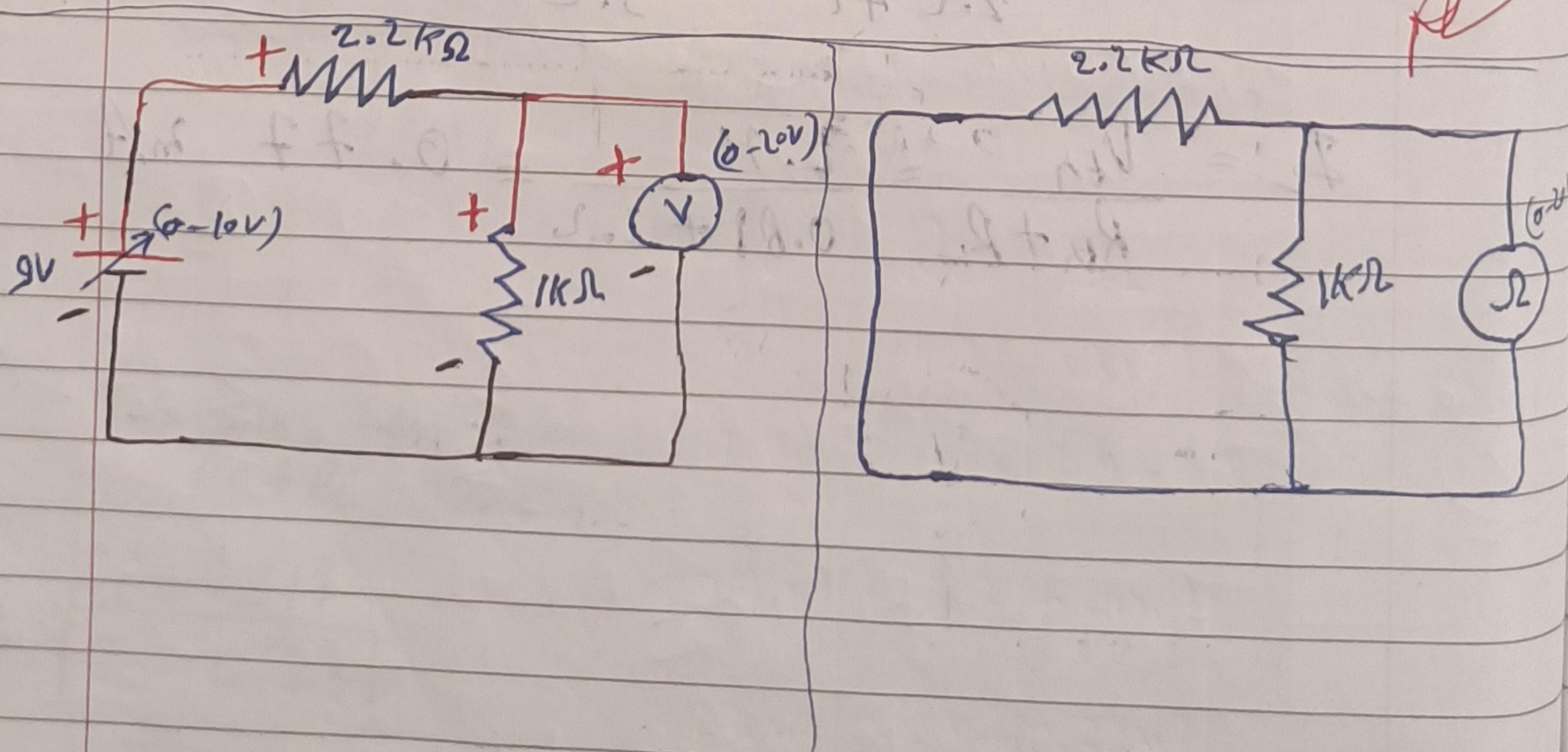Conclusion :- After performing this experiment we've found out that it's possible to simplify any linear circuit to an equivalent circuit with a voltage source and series resistance connected to the load resistance and the value we've calculated by formula was also as per value we got during experiment.



2 connections

PAGE NO.: 17

DATE: / /


Experiment - 5

Aim) To Verify Norton's theorem.

Apparatus Required:-


No	Equipment Name	Range	Quantity.
1	Voltmeter	(0-20V)	1
2	Ammeter	(0-200mA)	1
3	Resistance	1kΩ	1
4	Power Cols	2.2kΩ	2
5	Dc Power Supply (0-15V)		1
6	Patch cord		as per required

Circuit diagram

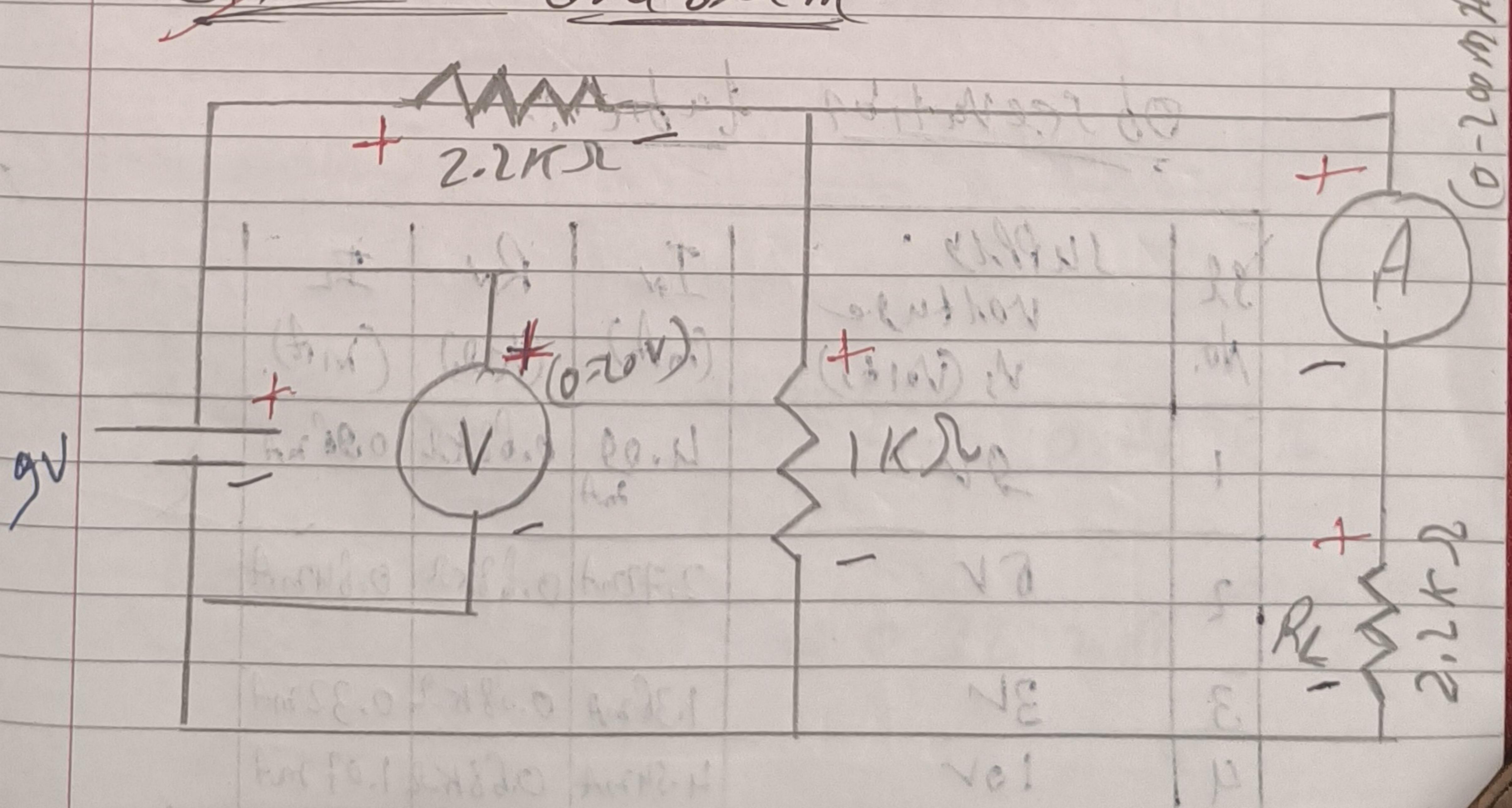


Case-1

for I_N

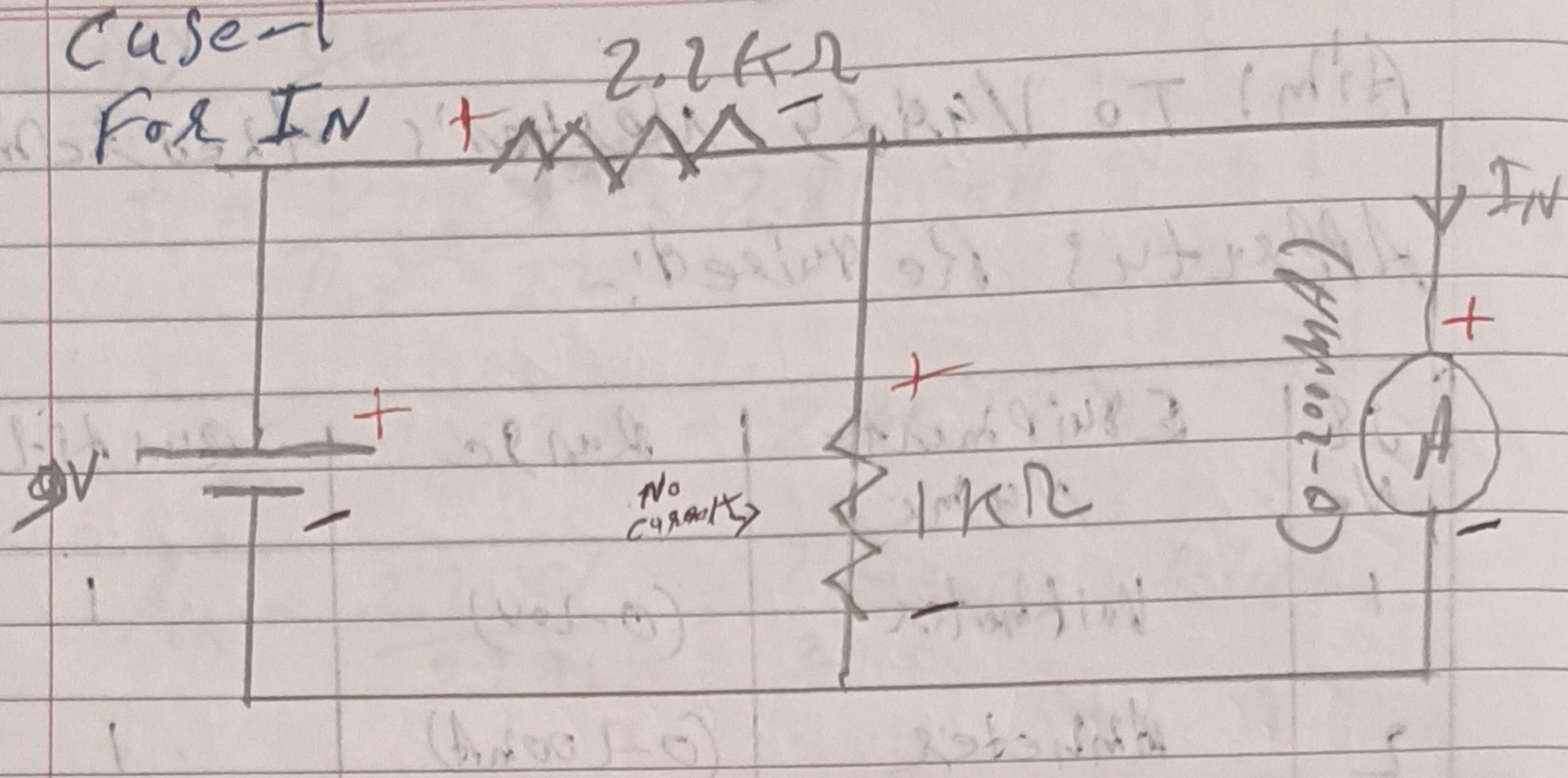

case-2

for R_N

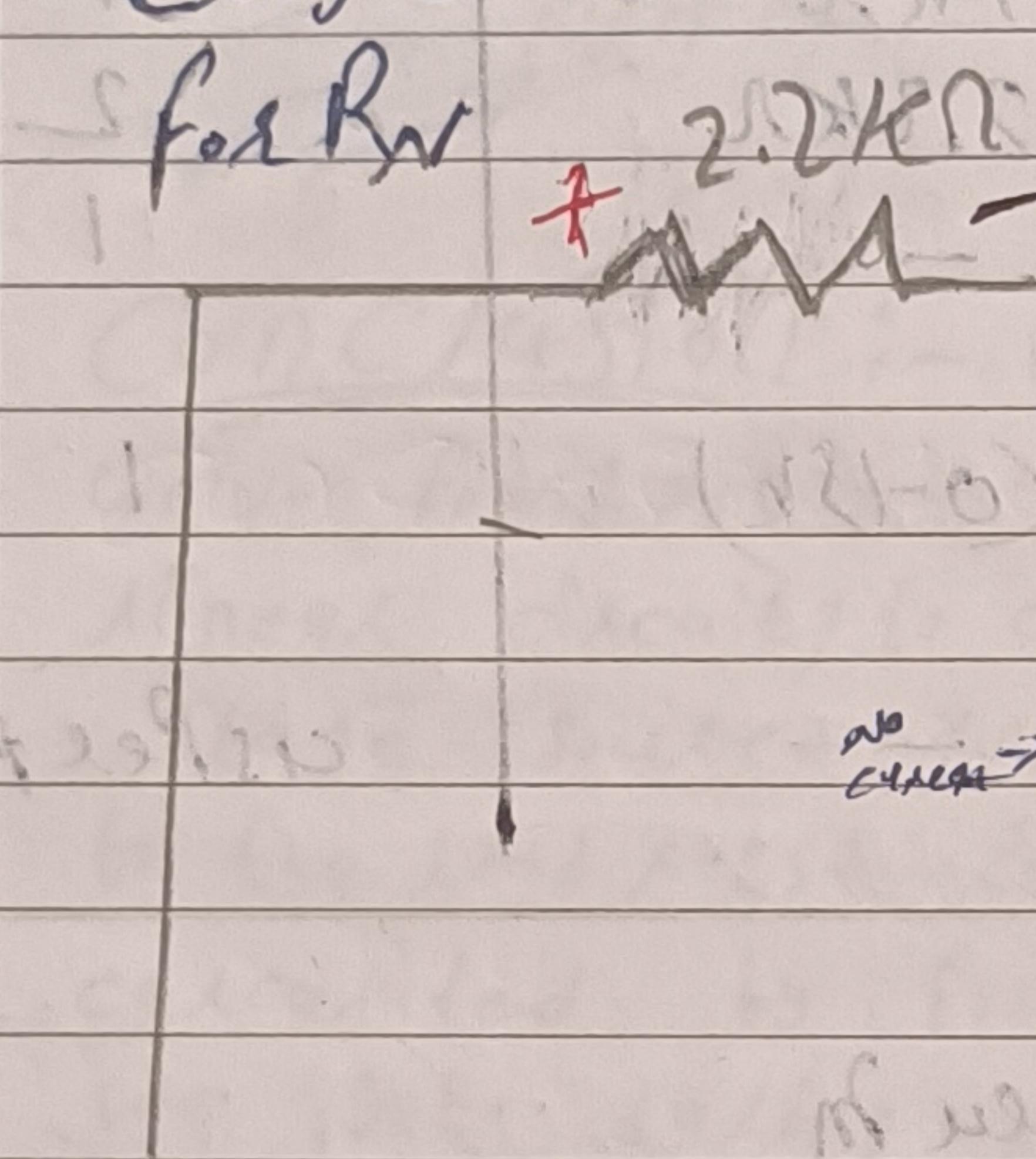

Observation table:-

SL No.	SUPPLY voltage V_s (V _{0.1} &S)	I_N (mA)	R_N (kΩ)	I_L (mA)
1	9V	4.09 mA	0.68 kΩ	0.98 mA
2	6V	2.72 mA	0.68 kΩ	0.64 mA
3	3V	1.36 mA	0.68 kΩ	0.32 mA
4	10V	4.54 mA	0.68 kΩ	1.07 mA

calculation

- For 9V

$$I_N = \frac{9}{2.2} = 4.09 \text{ mA}$$

$$R_N = \frac{2.2 \times 1}{2.2 + 1} = \frac{2.2 \times 1}{3.2} = 0.68 \text{ k}\Omega$$

$$I_L = \frac{4.09 \times 0.68}{0.68 + 2.2} = 0.96 \text{ mA}$$

- For 6V

$$I_N = \frac{6}{2.2} = 2.72 \text{ mA}$$

$$R_N = \frac{2.2 \times 1}{2.2 + 1} = 0.68 \text{ k}\Omega$$

$$I_L = \frac{2.72 \times 0.68}{0.68 + 2.2} = 0.84 \text{ mA}$$

- For 3V

$$I_N = \frac{3}{2.2} = 1.36 \text{ mA}$$

$$R_N = \frac{2.2 \times 1}{2.2 + 1} = \frac{2.2 \times 1}{3.2} = 0.68 \text{ k}\Omega$$

$$I_L = \frac{1.36 \times 0.68}{0.68 + 2.2} = 0.32 \text{ mA}$$

far 10 v

Notation

$$I_N = \frac{10}{2.2} = 4.54 \text{ mA}$$

$$R_N = \frac{2.2 \times 1}{2.2 + 1} = 0.68 \text{ k}\Omega$$

$$I_L = \frac{4.54 \times 0.68}{0.68 + 2.2} = 1.07 \text{ mA}$$

✓ P

Conclusion

Experiment - 6

PAGE NO.: 21

DATE: 17/1/2023

Aim:- To obtain resistance; capacitance, power and power factor of series RC circuit with phase AC supply using Phasor diagram.


Apparatus required:-

Sl No.	Equipment Name	Range	Quantity
1	Ac Voltmeter	(0-300V)	3
2	Ac Ammeter	(0-10A)	1
3	Single Phase Votac	(0-270V)	1
4	Ac Power Supply	(0-270V)	1
5	Resistance load	-	1
6	capacitive load	-	1
7	connecting wire	-	copper required

Circuit diagram

1-phase voltage

(0-10A)

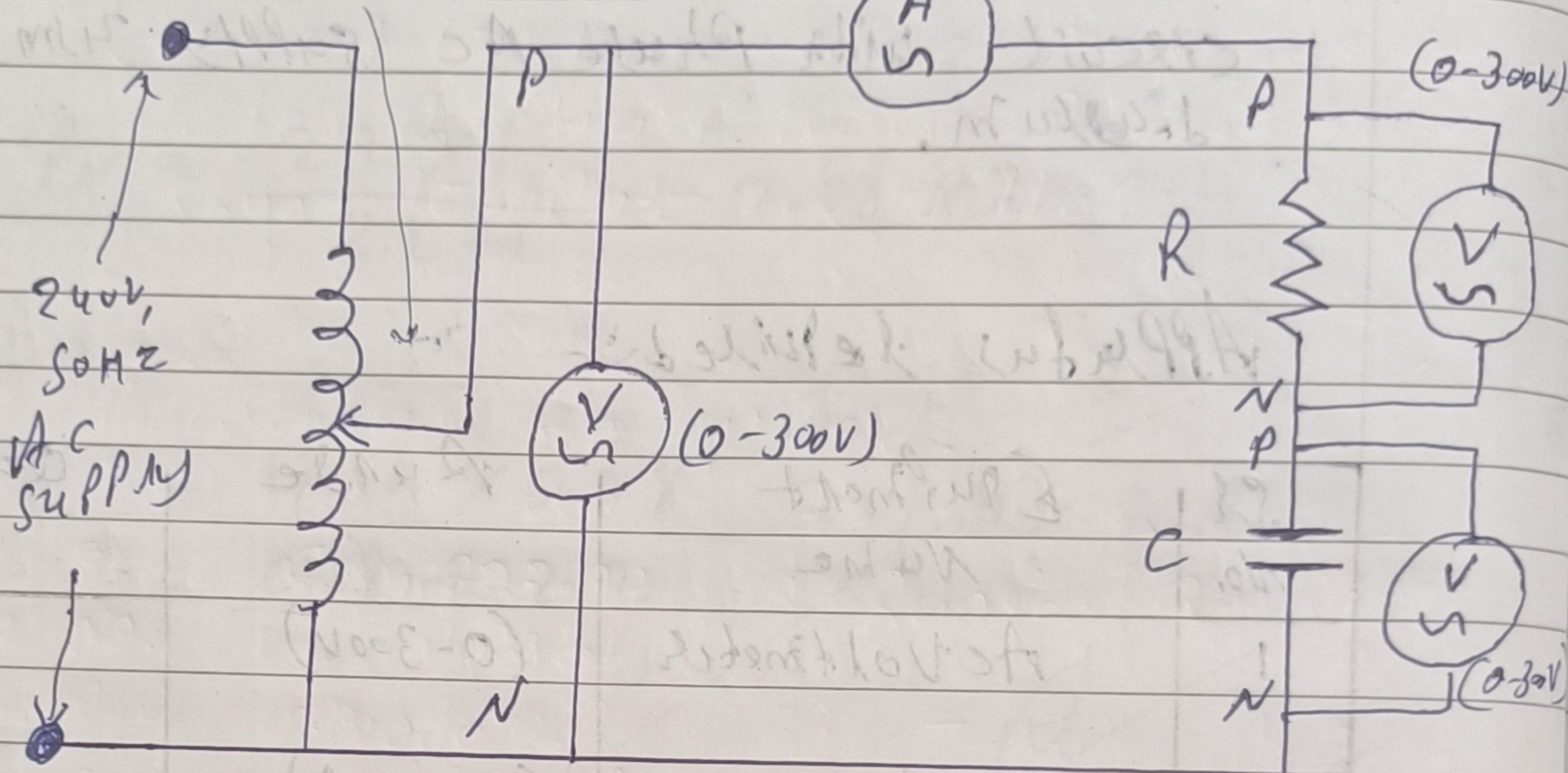

P = Phase

N = Neutral

Observation table

Sl No	SUPPLY VOLTAGE Vs (Volts)	CURRENT I (Amperes)	VOLTAGE ACROSS R-LOAD VR (Volts)	VOLTAGE ACROSS R-LOAD VR (Volts)
1.	100	0.4A	90V	32V
2	200	0.7A	186V	54V
3	150	0.6A	138V	42V

calculation table

Resistance $R = \frac{V_R}{I}$	capacitive Reactance $X_C = \frac{V_C}{I}$	Impedance $Z = \sqrt{R^2 + X_C^2}$	Power factor $\cos\phi = \frac{R}{Z}$	Power $P = VI \cos\phi$
250	80	262	0.95	38W
250	70	259	0.96	87W
285	77	295	0.96	128W

Conclusion:-

With increase in load power factor also increases.

Experiment - 7


Aim:- To observe half wave Rectified circuit (a) Half wave Rectifiers without filter (b) Half wave Rectifiers with Shunt capacitor filter.

Apparatus Required.

Sl No.	Equipment Name	Range	Quantity
1	Diode	-	1
2	Single Phase Ac Supply	230V	1
3	Dc Voltmeter	0-20V	1
4	Ac Voltmeter	0-200V	1
5	Ammeter	0-200mA	1
6	Oscilloscope	30 MHz	1
7	Patch code	-	as per required
8	Step down transformer (230-12V)		1

Circuit diagram

(a) Half wave Rectifier without filter

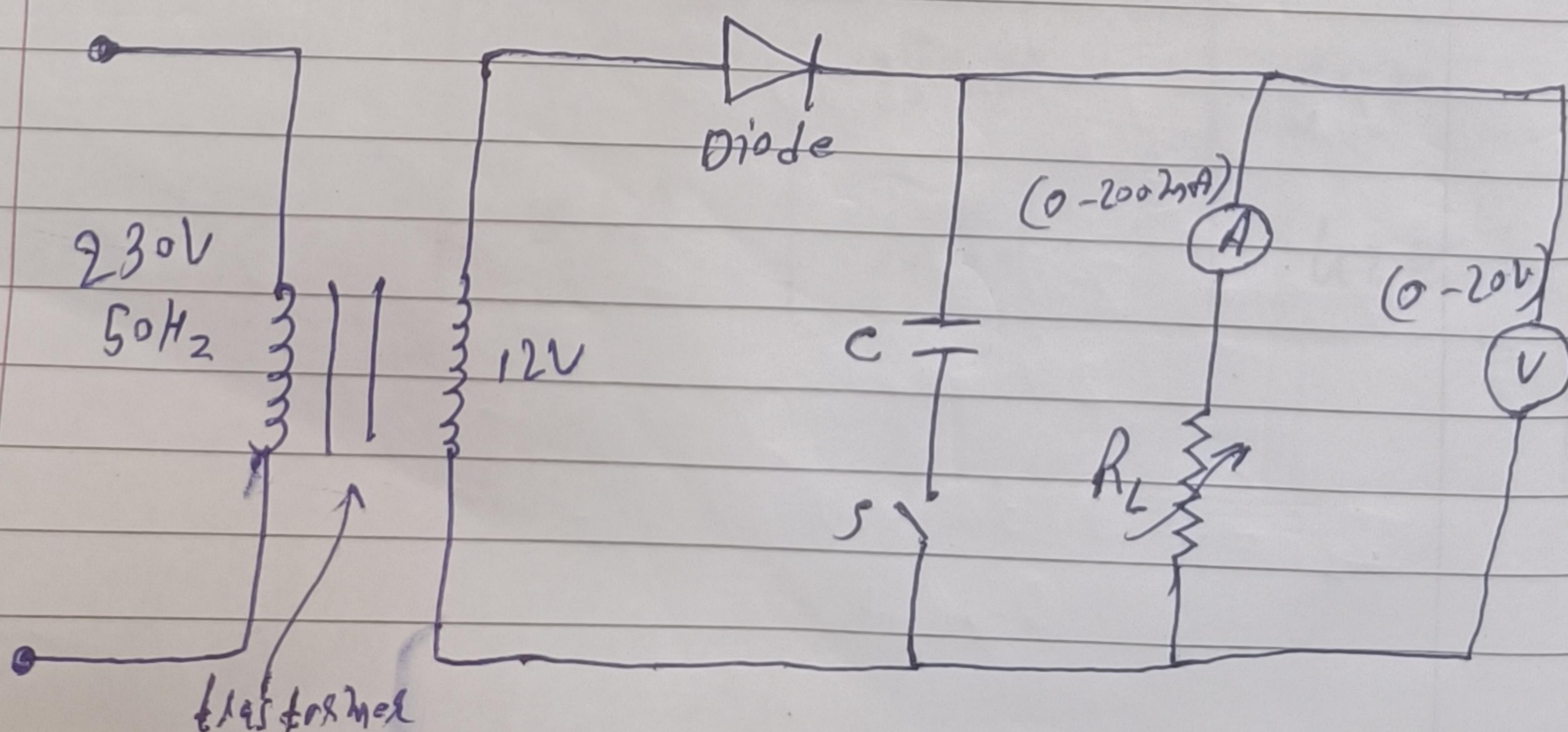


Observation Table

(a) Half wave Rectifier without filter

Sl No.	R_L	Input Ac Voltage V_{AC}	Output Ac Voltage V_{AC}	Dc current I_D	Output Dc Voltage V_{DC}	Efficiency Factor $\frac{V_{DC}}{V_{AC}}$
1	100	14.5	2.13	0.1	14.16	0.15
2	200	14.5	8.4	0.855	5.87	1.14
3	300	14.5	8.8	0.829	5.89	1.17
4	400	14.5	7.3	0.820	5.98	1.23
5	500	14.5	7.4	0.815	6.00	1.23
6	600	14.5	7.4	0.812	6.00	1.23
7	700	14.5	7.4	0.810	6.00	1.23

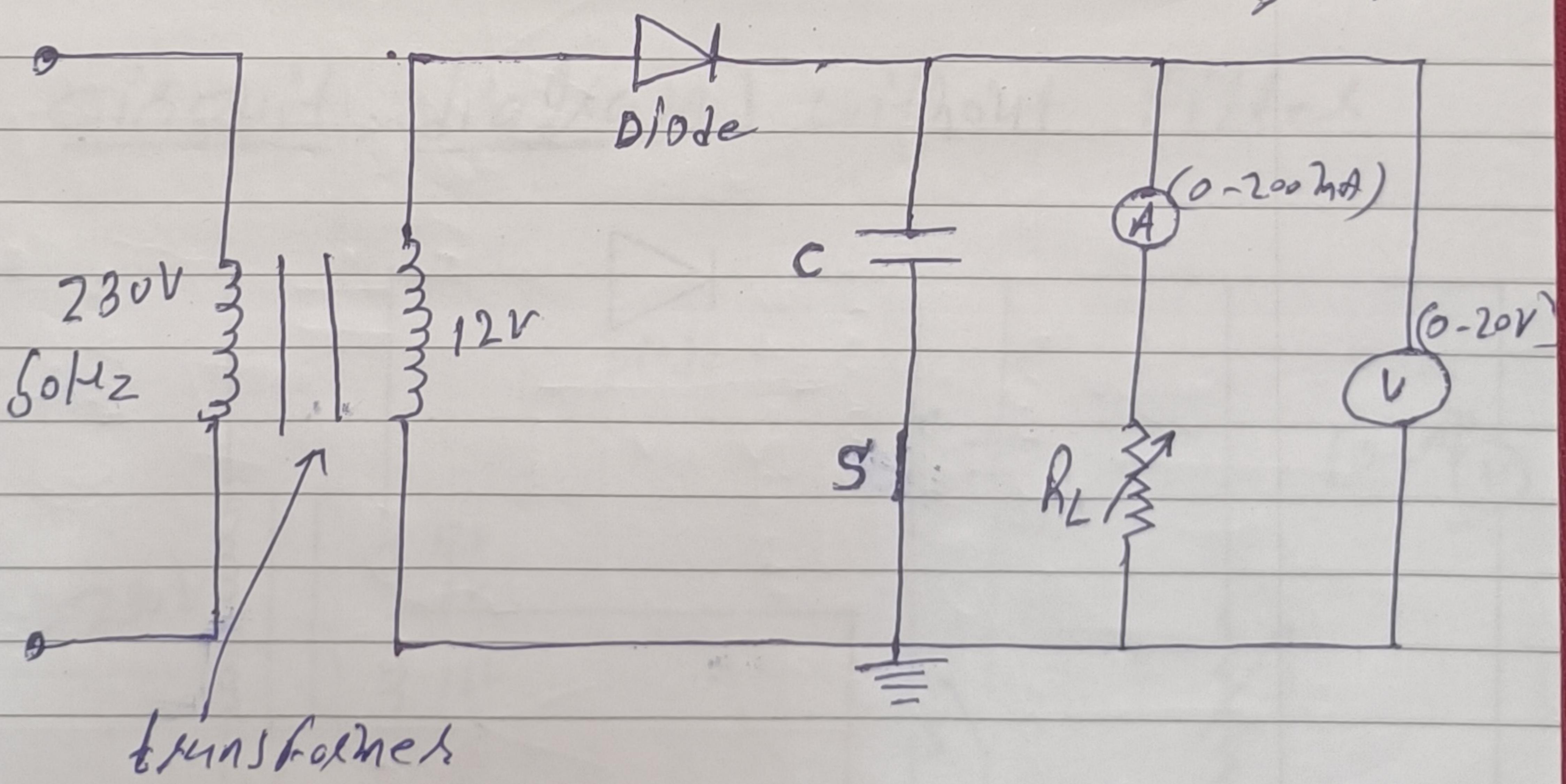(b) Half wave Rectified with capacitor filter.



Observation Table

Result (b) Half wave Rectifiers with capacitors filter

Sl. No.	R_L	Input Ac Voltage	Output Ac Voltage	Decay in ID	Output DC Voltage	Ripple Factor
		V_{AC}	V_{AC}		V_{DC}	$\frac{V_{AC}}{V_{DC}}$
1	100	14.5	8.4	0.01	19.8	0
2	200	14.5	4.4	76	2.2	0.71
3	300	14.5	3.7	52	10.3	0.42
4	400	14.5	3.17	40	12.1	0.30
5	500	14.5	2.7	33	13.2	0.29
6	600	14.5	2.7	28	14.14	0.19
7	700	14.5	2.4	24	14.8	0.18

Conclusion:-

Experiment - 8


PAGE NO.: 27
DATE: / /

Aim:- To observe full wave rectifier circuit with and without capacitor.

Apparatus Required:-

Sr No	Equipment Name	Range	Quantity
1	Diode	-	2
2	oscilloscope	30 MHz	1
3	Load Resistance	100 - 700 Ω	1
4	Power supply	230 V	1
5	Transformer (Stepdown)	230 - 12 V	1
6	Patch cable	-	As per Required
7	Voltmeter	0 - 20 V	1


Circuit diagram | without filter

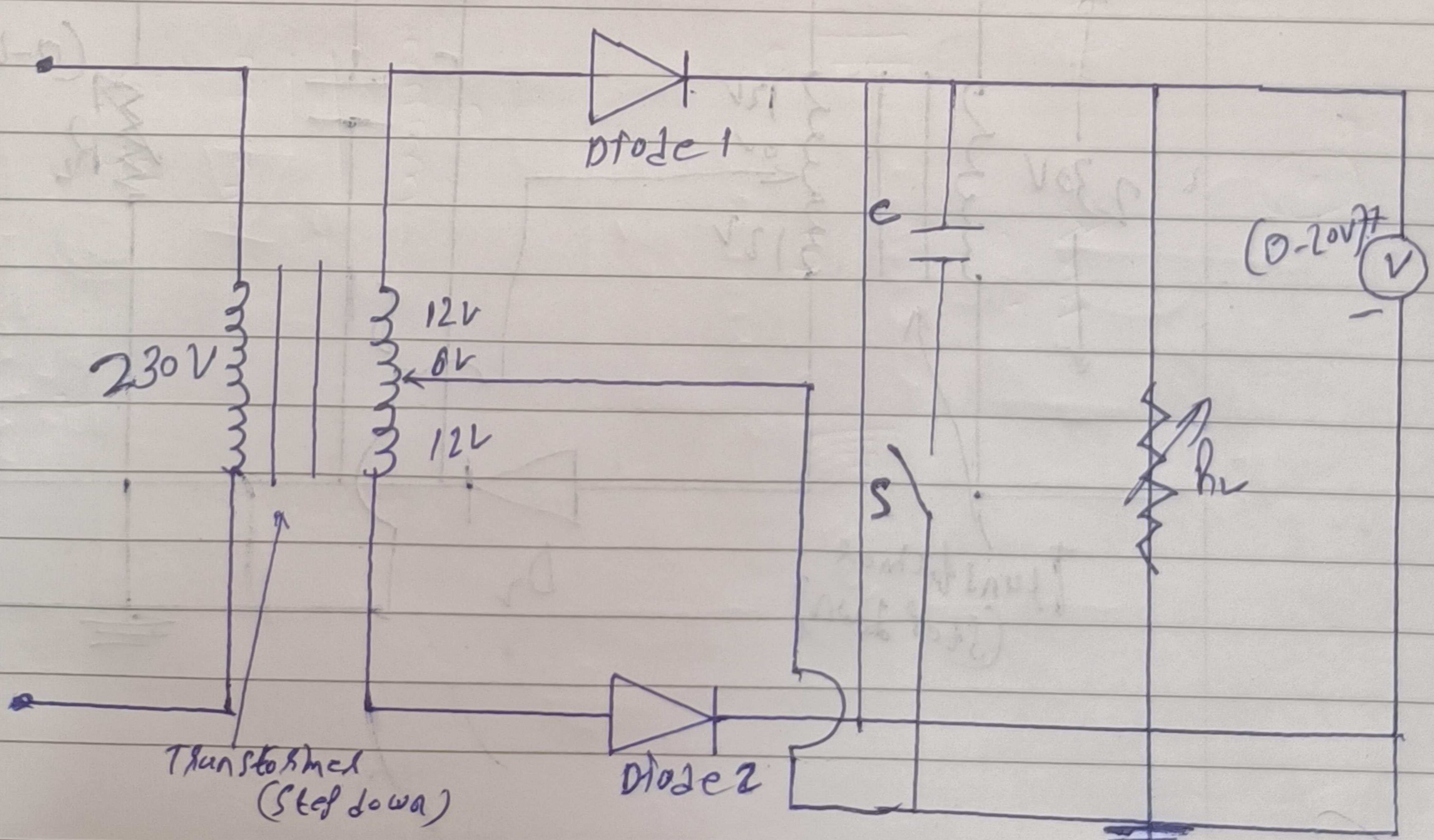

Observation table 1 without filter

Sl No	Load Resistance (R_L)	Output Voltage		Ripple factor $\frac{V_{AC}}{V_{DC}}$
		DC (V_{DC})	AC (V_{AC})	
1	100	12.1	5.7	0.47
2	200	13.5	6.4	0.47
3	300	14.1	6.6	0.46
4	400	14.4	6.8	0.47
5	500	14.6	6.9	0.47
6	600	14.7	7.0	0.47
7	700	14.8	7.0	0.47

Circuit diagram 1 with filter

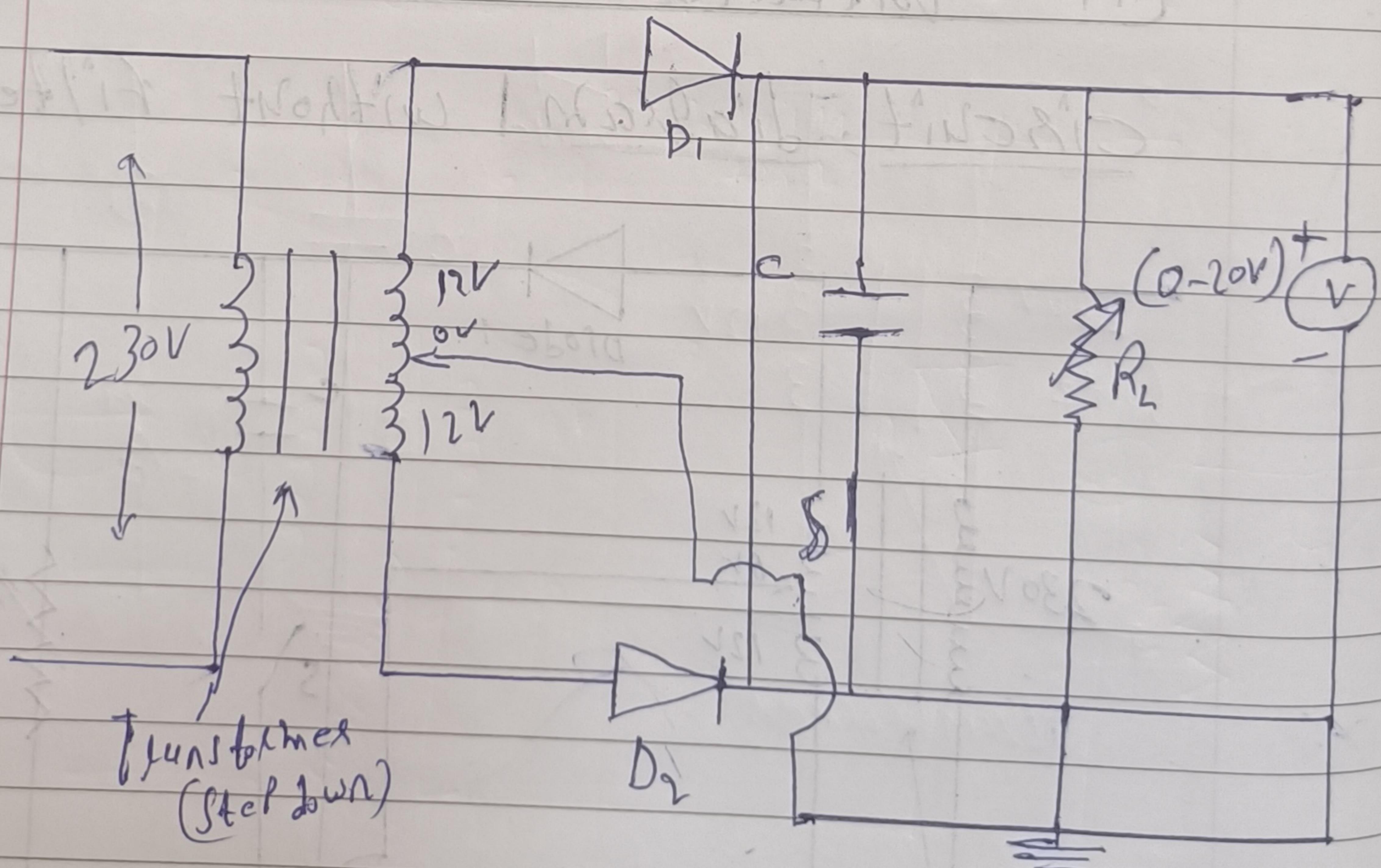

Observation - full wave rectifier with filter

SL	Load Resistance	AC (V _{AC})	DC V _{DC}	Ripple Factor
1	100	3.7	13.8	0.2
2	200	2.8	16.6	0.1
3	300	2.3	18.2	0.1
4	400	1.9	19.1	0.09
5	500	1.6	19.8	0.08
6	600	1.4	20.4	0.06
7	700	1.2	20.2	0.05

Conclusion :-

Experiment - 9


Aim:- To observe Response of Clipping Circuits using diodes.

Positive clipper and Negative clipper.


Apparatus:-

Sl No.	Equipment name	Range	Quantity
1	Diode	-	001 1N
2	Resistors	10kΩ	002 1
3	Single AC Supply	12V	001 1
4	Oscilloscope	13 MHz	001 1
5	Patch cable	-	As per required

Circuit Diagram | Positive clipper

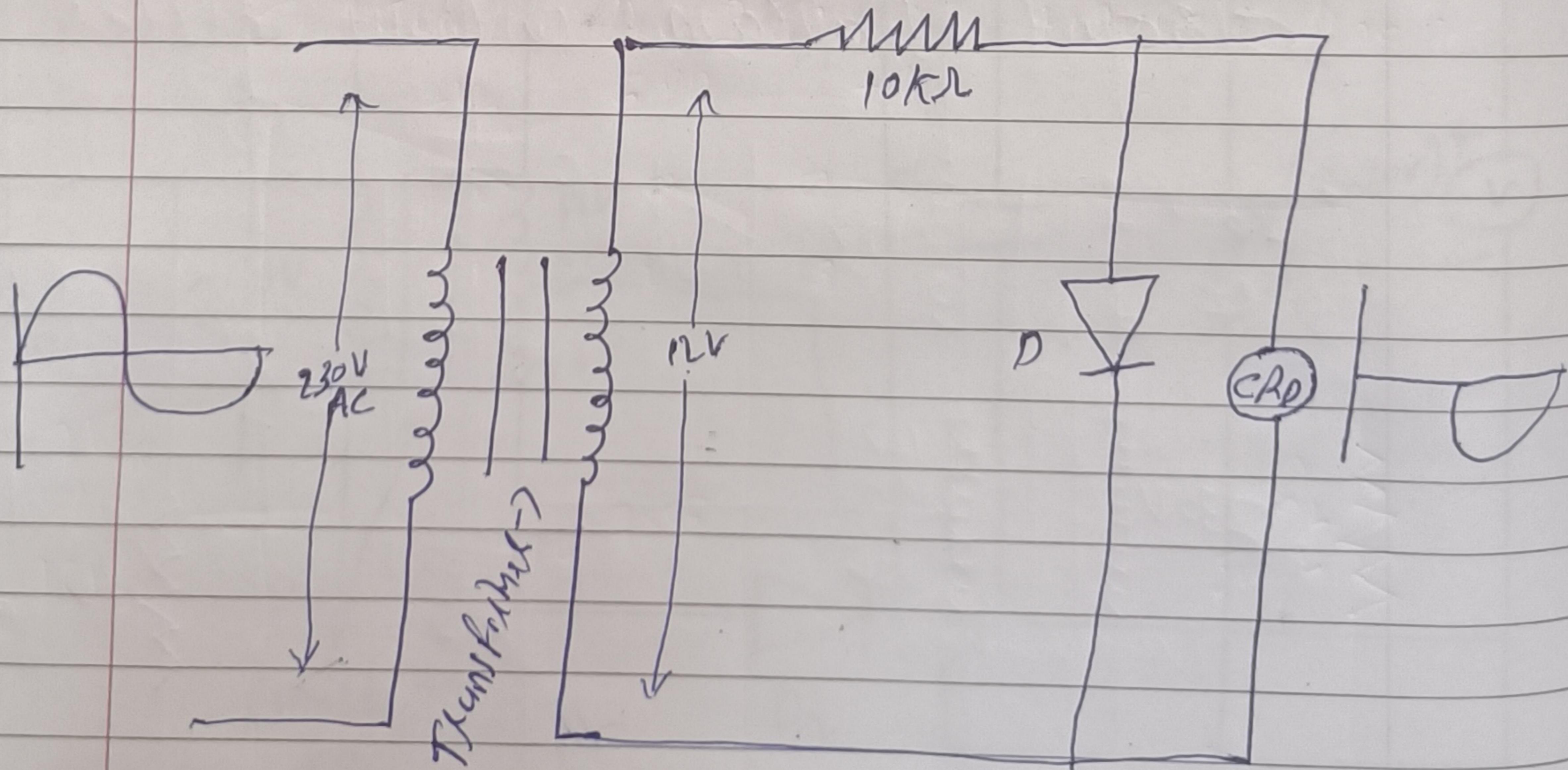

Negative clipped

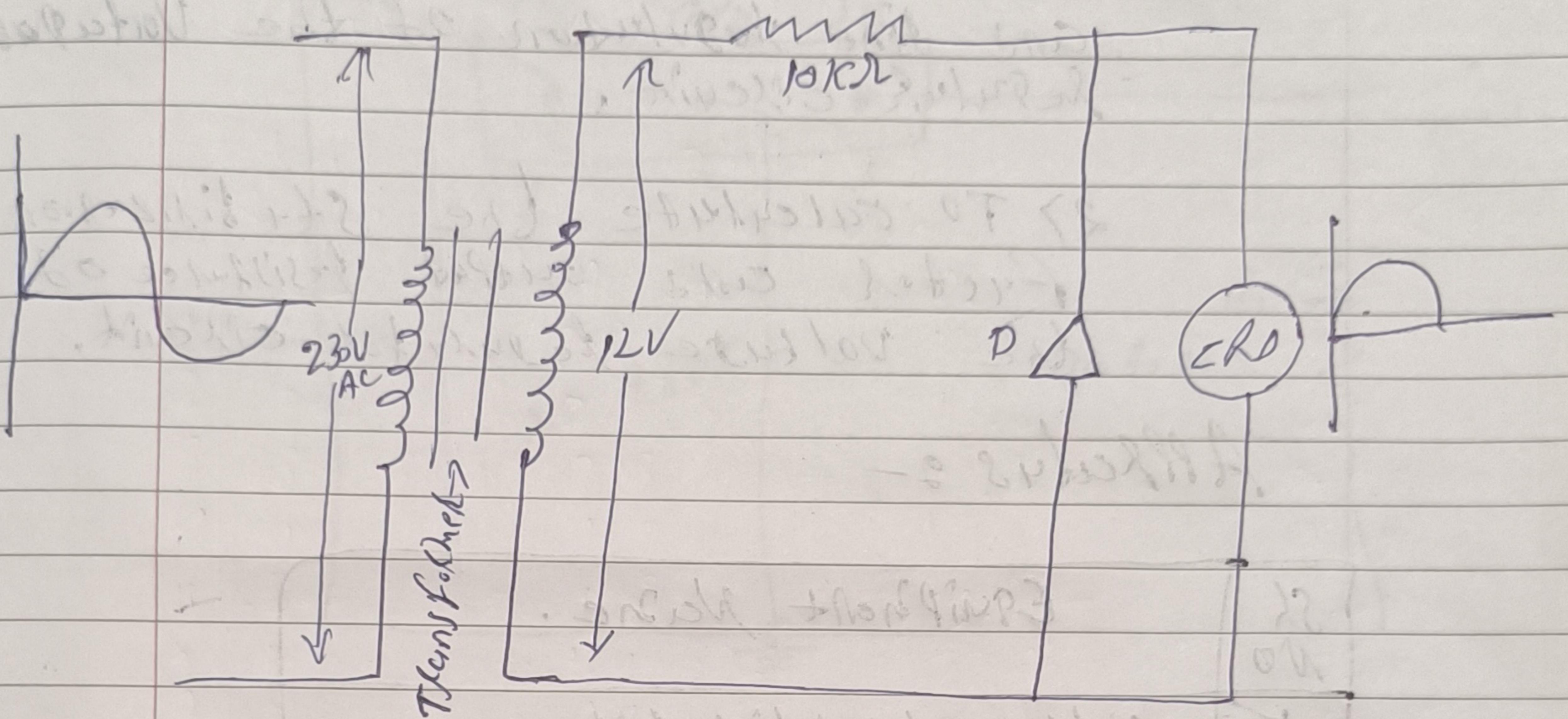

negative clipper

(inverted) output voltage

2V per division

Amplifier - 10000 times

at 2000

Experiment - 10

Aims— 1) To calculate the dead regulation and fine regulation of the Voltage regulator circuit.

2) To calculate the step-down factor and output resistance of the voltage regulator circuit.

Apparatus—

Sl No	Equipment Name.
1	Voltage regulating kit
2	Digital multimeter (V_{dc})
3	Connecting wires
4	Digital mill Ammeter (mA_{dc})

Circuit Diagram :- Figure 1 (line Regulator)


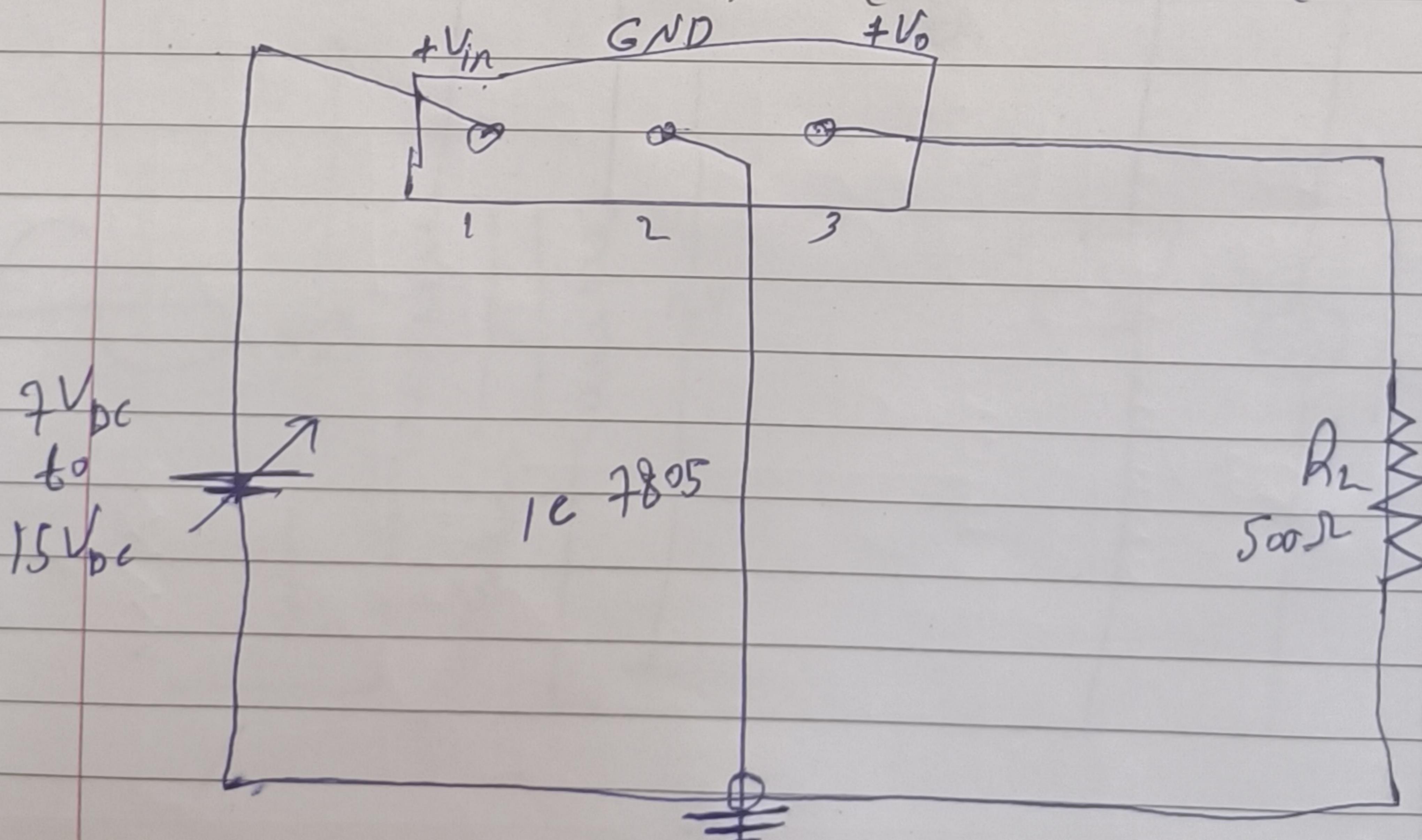


Figure 2 (Load Regulation)

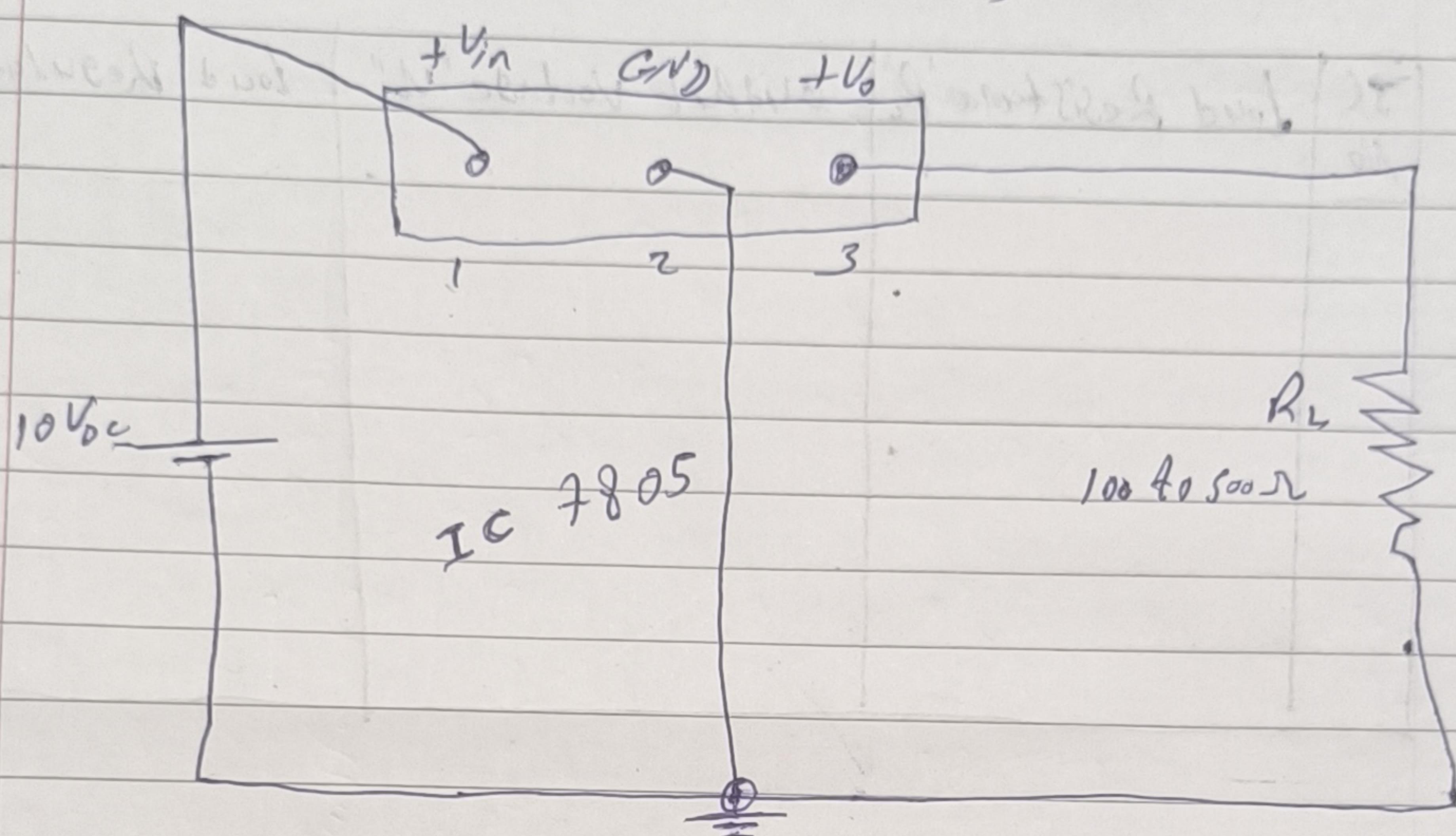

Observation table | Line Regulation ($R_L = 500\Omega$)

Sl No.	Input Voltage (V_{in})	Output Voltage (V_o)
	Input Voltage (V_{in})	

Load Regulation

No.	Load Resistance 'R'	Output Voltage "V"	Load Regulation
1	100 ohms	10.00 V	1%
2	200 ohms	9.80 V	1%
3	300 ohms	9.60 V	1%
4	400 ohms	9.40 V	1%
5	500 ohms	9.20 V	1%
6	600 ohms	9.00 V	1%
7	700 ohms	8.80 V	1%
8	800 ohms	8.60 V	1%
9	900 ohms	8.40 V	1%
10	1000 ohms	8.20 V	1%
11	1100 ohms	8.00 V	1%
12	1200 ohms	7.80 V	1%
13	1300 ohms	7.60 V	1%
14	1400 ohms	7.40 V	1%
15	1500 ohms	7.20 V	1%
16	1600 ohms	7.00 V	1%
17	1700 ohms	6.80 V	1%
18	1800 ohms	6.60 V	1%
19	1900 ohms	6.40 V	1%
20	2000 ohms	6.20 V	1%
21	2100 ohms	6.00 V	1%
22	2200 ohms	5.80 V	1%
23	2300 ohms	5.60 V	1%
24	2400 ohms	5.40 V	1%
25	2500 ohms	5.20 V	1%
26	2600 ohms	5.00 V	1%
27	2700 ohms	4.80 V	1%
28	2800 ohms	4.60 V	1%
29	2900 ohms	4.40 V	1%
30	3000 ohms	4.20 V	1%
31	3100 ohms	4.00 V	1%
32	3200 ohms	3.80 V	1%
33	3300 ohms	3.60 V	1%
34	3400 ohms	3.40 V	1%
35	3500 ohms	3.20 V	1%
36	3600 ohms	3.00 V	1%
37	3700 ohms	2.80 V	1%
38	3800 ohms	2.60 V	1%
39	3900 ohms	2.40 V	1%
40	4000 ohms	2.20 V	1%
41	4100 ohms	2.00 V	1%
42	4200 ohms	1.80 V	1%
43	4300 ohms	1.60 V	1%
44	4400 ohms	1.40 V	1%
45	4500 ohms	1.20 V	1%
46	4600 ohms	1.00 V	1%
47	4700 ohms	0.80 V	1%
48	4800 ohms	0.60 V	1%
49	4900 ohms	0.40 V	1%
50	5000 ohms	0.20 V	1%
51	5100 ohms	0.00 V	1%

Conclusion :-

(i) Load regulation is independent of load variation.

(ii) Current variation is 12%.

(iii) Output voltage is 0%.